2020 Digital IC Design

Homework 1: 4-bit binary adder-subtractor

1. Introduction

The binary adder-subtractor is a device that is capable of adding or subtracting elements. The following is a circuit which is used to add or subtract, depending on the control signal. Please implement a 4-bit binary adder-subtractor, the inputs adopts 2-complement expression.

2. Design Specifications:

2.1 Block Overview

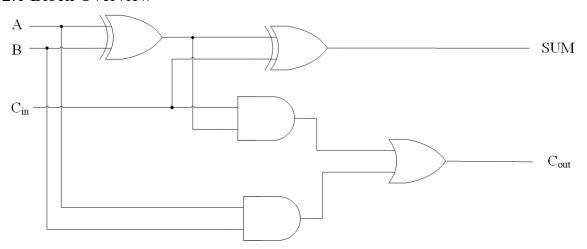


Fig 1. Full adder

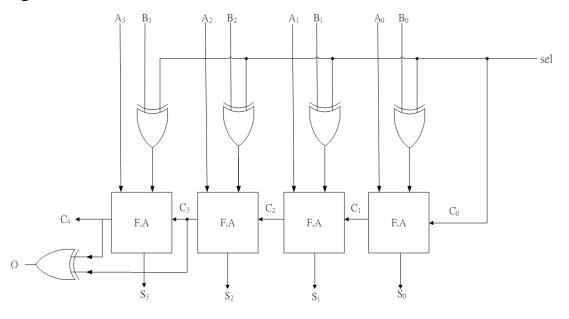


Fig 2. 4-bit binary adder-subtractor

2.2 I/O Interface

Signal Name	I/O	width	Description
sel	input	1	When sel=1, the circuit is a
			subtractor and when sel=0, the
			circuit becomes adder.
A	input	4	
В	input	4	
S	output	4	
О	output	1	Overflow

2.3 File Description

File Name	Description
AS.v	RTL code for using Verilog
AS_tb.v	Test bench for verifying design
cycloneii_atoms.v	Simulation library for gate-level simulation

2.4 Requirement

Please use dataflow description or structure description to design 4-bit binary adder-subtractor.

3. Scoring

3.1 Functional Simulation (pre-sim) [70%]

All of the results should be generated correctly. If all of the results are correct, you will get the following message in ModelSim simulation.


```
# 504 data is correct
# 505 data is correct
# 506 data is correct
# 507 data is correct
# 508 data is correct
# 509 data is correct
# 510 data is correct
# 511 data is correct
# 512 data is correct
# 512 data is correct
# All data have been generated successfully!
# Break in Module AS_tb at E:/DIC_HW/DIC_HW1/AS_tb.v line 63
VSIM 43>
```

3.2 Gate-Level Simulation (post-sim) [30%]

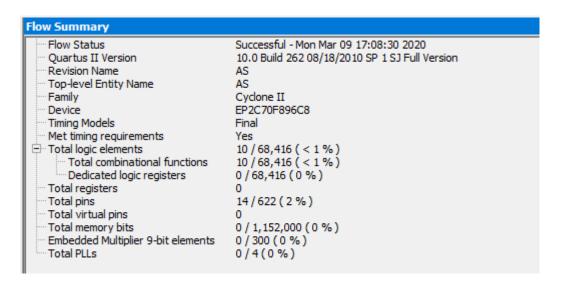3.2.1 Synthesis

Your code should be synthesizable. After synthesizing with

Quartus, a file named AS.vo will be obtained.



Device: Cyclone II EP2C70F896C8

3.2.2 Simulation

All of the results should be generated correctly by using AS.vo, and you will get the following message in ModelSim simulation.

```
# 503 data is correct
# 504 data is correct
# 505 data is correct
# 506 data is correct
# 507 data is correct
# 508 data is correct
# 509 data is correct
# 510 data is correct
# 511 data is correct
# 512 data is correct
# 4 512 data is correct
# 514 data have been generated successfully!
# Break in Module AS_tb at E:/DIC_HW/DIC_HWI/AS_tb.v line 63
```

3.3 Performance [0 %]

The performance is scored by the logic elements you used and the simulation time in post-sim. The scoring equation is (Total logic elements + total memory bit+ 9*embedded multiplier 9-bit element) \times (longest gate-level simulation time with ns). (The smaller the better).

3.4 Note

You can modify clock cycle in the file named AS_tb in post-sim.

```
`timescale 10ns / 1ps
`define CYCLE 5
    define A_dat "./A.txt"
    define B_dat "./B.txt"
    define O_dat "./O.txt"
    define SUM_dat "./SUM.txt"
    module AS_tb;
```

4. Submission

4.1 Submitted files

You should classify your files into three directories and compressed to .zip format. The naming rule is HW1 studentID name.zip.

	RTL category			
*.V	All of your Verilog RTL code			
	Gate-Level category			
*.vo	Gate-Level netlist generated by Quartus			
*.sdo	SDF timing information generated by			
	Quartus			
	Documentary category			
*.pdf	The report file of your design (in pdf).			

4.2 Report file

Please follow the spec of report. You are asked to describe how the circuit is designed as detailed as possible, and the summary results and minimum CYCLE in post-sim are necessary.

4.3 Please submit your .zip file to folder HW1 in the moodle.

Deadline: 2020-04-14 23:55

5. If you have any problem, please contact by the TA by email: weiting84610@gmail.com 陳威廷

f74044088@gs.ncku.edu.tw 倪祺婷